

**FACULTY OF SCIENCE AND TECHNOLOGY**  
**Assignment (Laboratory) Coversheet**

Student ID number	U3312590
Student Name	Jasmine Bajracharya
Unit name	Introduction to Computer Engineering
Unit number	10096
Name of lecturer/tutor	Dr. Julio Romero
Assignment topic	HDL and Microprocessors
Due date	2 <sup>nd</sup> November, 2025
Word Count	1404


***You must keep a photocopy or electronic copy of your assignment.***

**Student declaration**

I certify that the attached assignment is my own work. Material drawn from other sources has been appropriately and fully acknowledged as to author/creator, source and other bibliographic details. Such referencing may need to meet unit-specific requirements as to format and style.

I give permission for my assignment to be copied, submitted and retained for the electronic checking of plagiarism.

**Signature of student:**

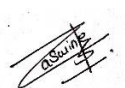

**Date: 30<sup>th</sup> October 2025**

(Students submitting work electronically can type their name in the space for signature above, but must produce a signed copy of this coversheet on request.)

**Date of submission: 30<sup>th</sup> October 2025**

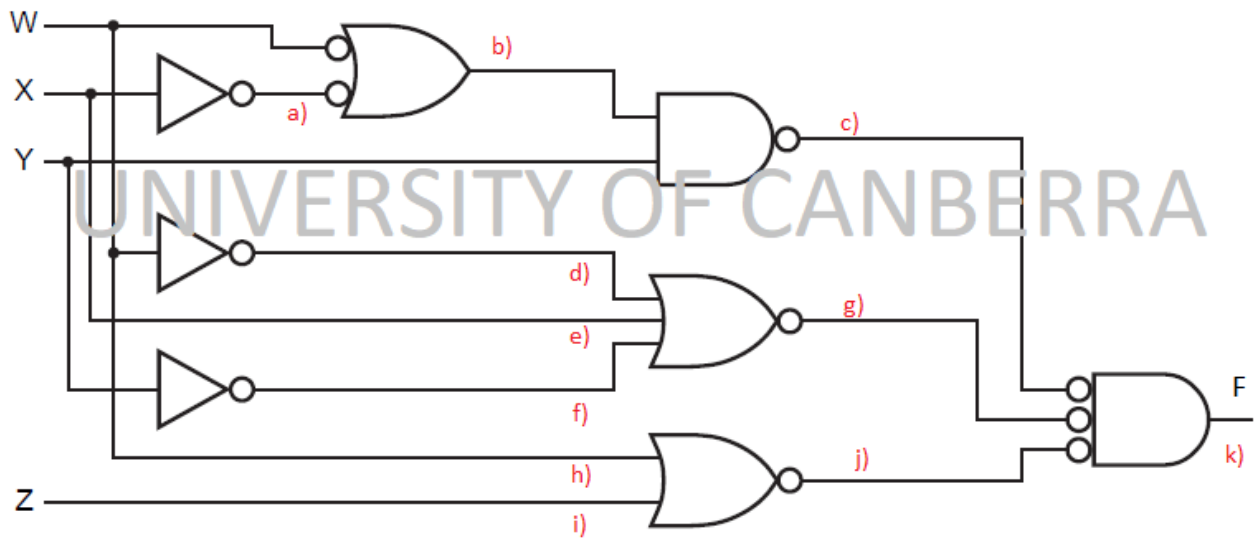


Figure 1: Boolean Circuit for Laboratory Week 12

### 1. Boolean Expression Derivation from Circuit (20 marks)

Derive the Boolean expression that describes the circuit shown in Figure 1. Show your steps in each branch of the circuit given.

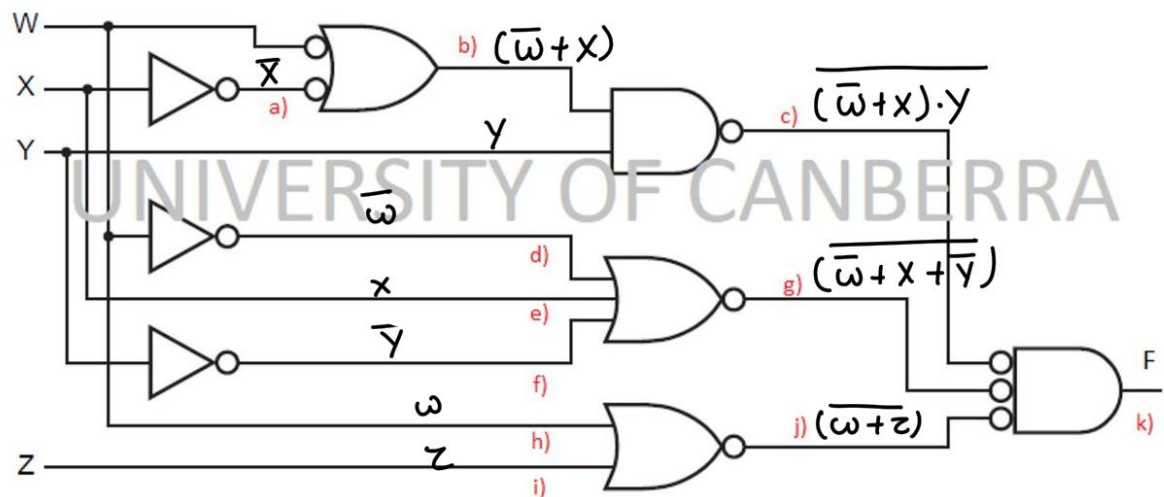


Figure 1: Boolean Circuit for Laboratory Week 12

$$F = \overline{\overline{(W+X) \cdot Y} \cdot \overline{(W+X+Y)}} \cdot \overline{(W+Z)}$$

$$F = \overline{\overline{(W+X) \cdot Y} \cdot \overline{(W+X+Y)}} \cdot \overline{(W+Z)}$$

Here, we have for each intermediate expression we get,

$$a = \bar{X}$$

$$b = \bar{W} + X = \overline{W \cdot \bar{X}}$$

$$c = \overline{Y \cdot W \bar{X}}$$

$$d = \bar{W}$$

$$e = X$$

$$f = \bar{Y}$$

$$g = \overline{\bar{W} + X + \bar{Y}}$$

$$h = W$$

$$i = Z$$

$$j = (\bar{W} + \bar{Z})$$

$$k = \overline{Y \cdot W \bar{X} + \bar{W} + X + \bar{Y} + \bar{W} + \bar{Z}}$$

## 2. Boolean Expression Simplification Using Theorems (10 marks)

On simplification, the expression is given as:

$$F = \overline{Y \cdot W \bar{X} + \bar{W} + X + \bar{Y} + \bar{W} + \bar{Z}}$$

$$F = \overline{Y \cdot W \bar{X}} \cdot \overline{\bar{W} + X + \bar{Y}} \cdot \overline{\bar{W} + \bar{Z}} \quad [\text{Applying De - morgan's theorem}]$$

$$F = Y \cdot \bar{W} \bar{X} \cdot (\bar{W} + X + \bar{Y}) \cdot (W + Z) \quad [\text{Applying tautology}]$$

$$F = Y(\bar{W} + \bar{X}) \cdot (\bar{W} + X + \bar{Y}) \cdot (W + Z) \quad [\text{Applying De - Morgan's law}]$$

$$F = Y(\bar{W} + X) \cdot (\bar{W} + X + \bar{Y}) \cdot (W + Z) \quad [\text{Applying tautology}]$$

$$F = Y(\bar{W} + X + \bar{Y}) \cdot (W + Z) \bar{W} + Y \cdot (\bar{W} + X + \bar{Y}) \cdot (W + Z) X \quad [\text{Applying distribution law}]$$

$$F = Y(W + Z)\overline{W}.\overline{W} + Y(W + Z)X.\overline{W} + Y(W + Z)\overline{W}.\overline{Y} + Y(\overline{W} + X + \overline{Y}).(W + Z)X \quad [\text{Applying idempotent law}]$$

$$F = Y(W + Z)\overline{W} + Y(W + Z)X.\overline{W} + 0 + Y(\overline{W} + X + \overline{Y}).(W + Z)X \quad [\text{Applying complement law}]$$

$$F = Y(W + Z)\overline{W} + Y(W + Z)X.\overline{W} + Y(\overline{W} + X + \overline{Y}).(W + Z)X \quad [\text{Applying identity law}]$$

$$F = Y(W + Z)\overline{W} + Y(\overline{W} + X + \overline{Y}).(W + Z)X \quad [\text{Applying absorption law}]$$

$$F = YW\overline{W} + Y\overline{W}Z + Y(\overline{W} + X + \overline{Y}).(W + Z)X \quad [\text{Applying distribution law}]$$

$$F = 0 + Y\overline{W}Z + Y(\overline{W} + X + \overline{Y}).(W + Z)X \quad [\text{Applying complement law}]$$

$$F = Y\overline{W}Z + Y(\overline{W} + X + \overline{Y}).(W + Z)X \quad [\text{Applying identity law}]$$

$$F = Y\overline{W}Z + Y(W + Z)X\overline{W} + Y(W + Z)XX + Y(W + Z)X.\overline{Y} \quad [\text{Applying distribution law}]$$

$$F = Y\overline{W}Z + Y(W + Z)X\overline{W} + Y(W + Z)X + Y(W + Z)X.\overline{Y} \quad [\text{Applying idempotent law}]$$

$$F = Y\overline{W}Z + Y(W + Z)X\overline{W} + Y(W + Z)X + 0 \quad [\text{Applying complement law}]$$

$$F = Y\overline{W}Z + Y(W + Z)X\overline{W} + Y(W + Z)X \quad [\text{Applying identity law}]$$

$$F = Y\overline{W}Z + Y(W + Z)X \quad [\text{Applying absorption law}]$$

$$F = \overline{W}YZ + WXY + XYZ \quad [\text{Applying distribution law}]$$

$$F = \overline{W}YZ + WXY + XYZ$$

### 3. Boolean Expression Simplification Using Karnaugh Maps (10 marks)

The truth table for the above circuit is given as:

W	X	Y	Z	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0

1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

Now, using Karnaugh map for the simplification of the expression, we get:

	$\bar{Y} \bar{Z}$	$\bar{Y} Z$	$YZ$	$Y \bar{Z}$
$\bar{W} \bar{X}$	0	0	1	0
$\bar{W} X$	0	0	1	0
$WX$	0	0	1	1
$W \bar{X}$	0	0	0	0

On grouping the rows for 1's we get:

$$F = \bar{W}YZ + WXY$$

The results from the simplification and Karnaugh map are different due to the redundancy in the terms in the manually simplified expression. The results are, however, equivalent.

#### 4. VHDL Code representation SA (20 marks)

From simplification obtained above, and using the structural approach, the code representation using structural approach is given as:

considering , W -> IN1, X -> IN2, Y-> IN3, Z-> IN4 and F -> OUT

```
entity Logic is
    port(IN1, IN2, IN3, IN4 : in bit; OUT5: out bit);
architecture LogicCircuit of Circuit is
    component NOT_gate is
        port(A:in bit;X:out bit);
    end component NOT_GATE;

    component AND_gate3 is
        port(A, B,C: in bit; X:out bit);
    end component AND_GATE;

    component OR_gate3 is
        port (A,B, C : in bit; X:out bit);
    end component OR_GATE;
```

```
signal OUT1, OUT2, OUT3, OUT4: bit;
begin
    G1: NOT_gate port map( A=>IN1, X=>OUT1);
    G2: And_gate3 port map (A=>IN1, B=>IN2, C=>IN3, X=>OUT2)
    G3: And_gate3 port map (A=>IN2, B=>IN3, C=>IN4, X=>OUT3)
    G4: And_gate3 port map (A=>IN2, B=>OUT1, C=>IN4, X=>OUT4)
    G5: OR_gate3 port map (A=> OUT2 , B=>OUT3, C=>OUT4, X=>OUT5)
end architecture LogicCircuit;
```

## 5. VHDL Code representation DF (20 marks)

From simplification obtained above, using the Data Flow approach, we get the code as:

```
entity Logic is
    port(
        W: in STD_LOGIC;
        X: in STD_LOGIC;
        Y : in STD_LOGIC;
        Z : in STD_LOGIC;
        F : out STD_LOGIC;
    );
End Logic;
Architecture Behavioral of Logic is
begin
    F<= (W and X and Y) or (X and Y and Z) or (not W and Y and Z)
end Behavioral;
```

## 6. VHDL Implementation (20 marks)

From simplification obtained above, and using the data flow approach,

**6.1** Correct structure of the code written in Vivado. It includes proper I/O mapping.

The code written in Vivado is as follows:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tute_12 is
    port(
        W: in STD_LOGIC;
        X: in STD_LOGIC;
        Y : in STD_LOGIC;
        Z : in STD_LOGIC;
        F : out STD_LOGIC;
    );
```

```
);  
End tute_12;  
Architecture Behavioral of tute_12 is  
begin  
    F<= (W and X and Y) or (X and Y and Z) or (not W and Y and Z)  
end Behavioral;
```


Similarly, the testbench for the above is written as:

```
Library IEEE;  
Use IEEE.STD_LOGIC_1164.ALL;  
  
Entity tb_and_gate is  
End tb_and_gate;  
  
architecture behavior of tb_and_gate is  
    Signal A, B, Y; STD_LOGIC;  
Begin  
    uut.entity work.tute_12  
        port map(  
            W => W,  
            X => X,  
            Y => Y,  
            Z => Z,  
            F => F);  
  
    -- Test process  
process  
begin  
    W <= '0' ; X <= '0' ; Y <= '0' ; Z<='0' wait for 10 ns;  
    W <= '0' ; X <= '0' ; Y <= '0' ; Z<='1' wait for 10 ns;  
    W <= '0' ; X <= '0' ; Y <= '1' ; Z<='0' wait for 10 ns;  
    W <= '0' ; X <= '0' ; Y <= '1' ; Z<='1' wait for 10 ns;  
    W <= '0' ; X <= '1' ; Y <= '0' ; Z<='0' wait for 10 ns;  
    W <= '0' ; X <= '1' ; Y <= '0' ; Z<='1' wait for 10 ns;  
    W <= '0' ; X <= '1' ; Y <= '1' ; Z<='0' wait for 10 ns;  
    W <= '0' ; X <= '1' ; Y <= '1' ; Z<='1' wait for 10 ns;  
    W <= '1' ; X <= '0' ; Y <= '0' ; Z<='0' wait for 10 ns;  
    W <= '1' ; X <= '0' ; Y <= '0' ; Z<='1' wait for 10 ns;  
    W <= '1' ; X <= '0' ; Y <= '1' ; Z<='0' wait for 10 ns;  
    W <= '1' ; X <= '0' ; Y <= '1' ; Z<='1' wait for 10 ns;  
    W <= '1' ; X <= '1' ; Y <= '0' ; Z<='0' wait for 10 ns;  
    W <= '1' ; X <= '1' ; Y <= '0' ; Z<='1' wait for 10 ns;  
    W <= '1' ; X <= '1' ; Y <= '1' ; Z<='0' wait for 10 ns;  
    W <= '1' ; X <= '1' ; Y <= '1' ; Z<='1' wait for 10 ns;  
    Wait;
```


end process;  
end behavior;
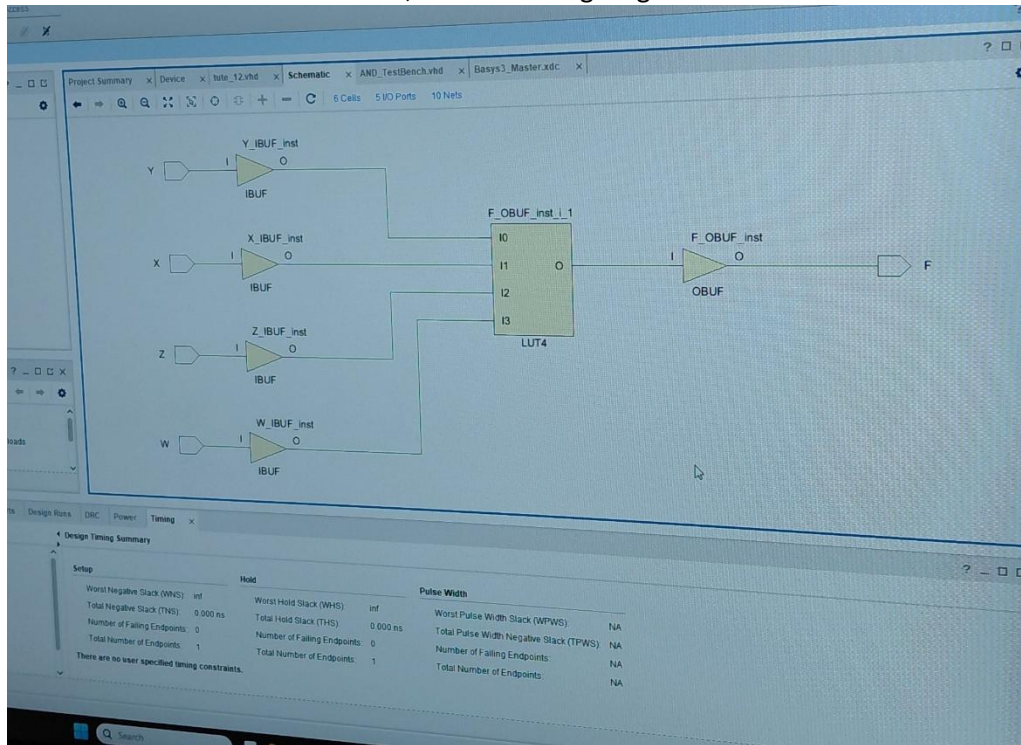
## 6.2 Correct simulation of the circuit in Vivado (time diagram).

The circuit was simulated, and the timing diagram was obtained as:





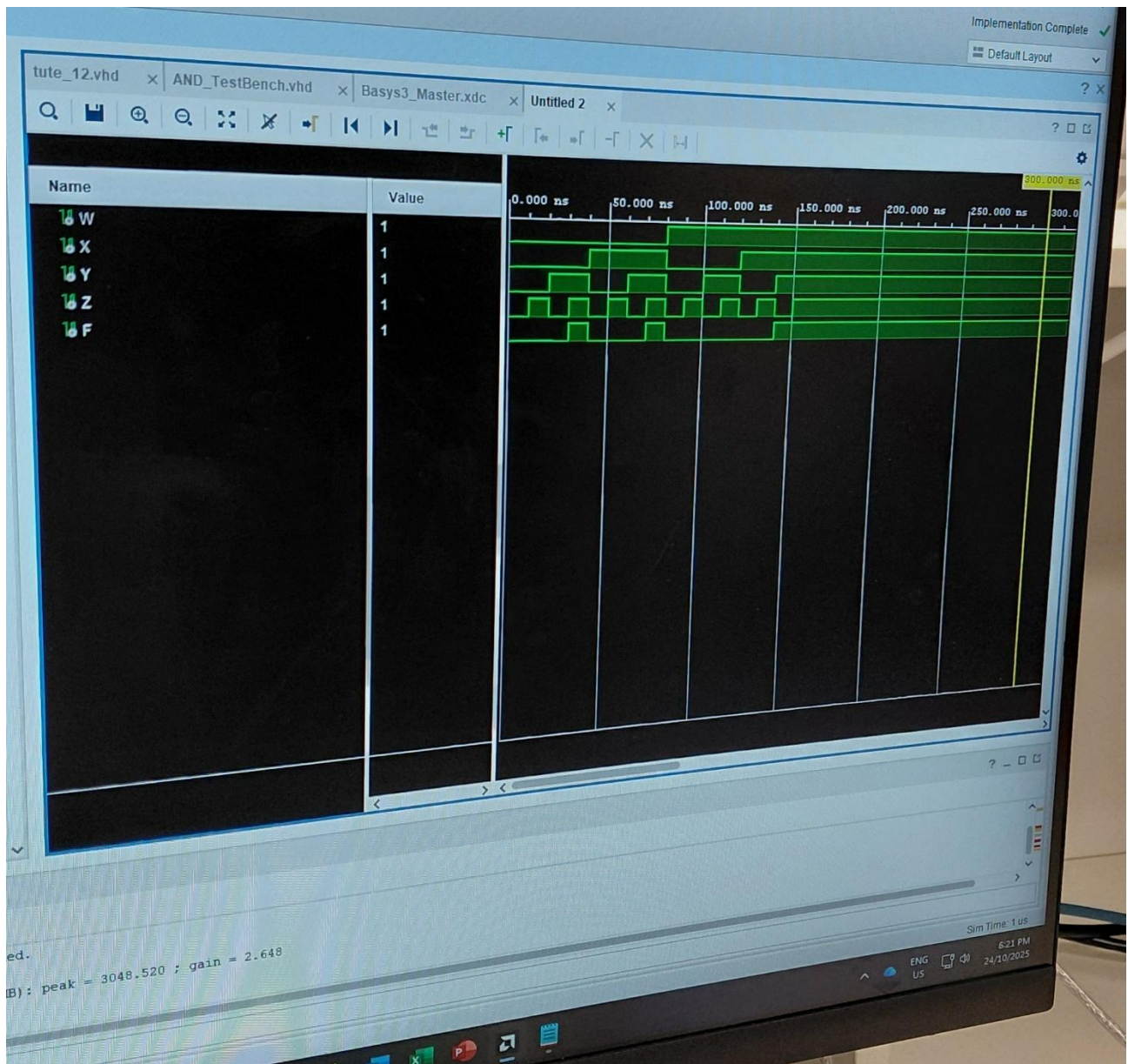

*\*Note: The simulation video (timing diagram) can be accessed through the file [timing\\_diagram\\_video/timing\\_diagram.mp4](#)*

**6.3** Correct functioning of the FPGA by verifying that your circuit works as intended using a truth table.

The truth table for the circuit is as follows:


W	X	Y	Z	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0

**UNIVERSITY OF CANBERRA**  
**INTRODUCTION TO COMPUTER ENGINEERING (8223/10096)**  
**TUTORIAL WEEK 12 Assignment**



0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1
1	1	1	1	1

 The FPGA implementation of the circuit is given as:



*\*Note: The FPGA implementation can be accessed through the file : [FPGA\\_video/FPGA\\_implementation.mp4](#)*

## REFERENCES

- [1] Floyd, Th.L. Digital Fundamentals, Pearson, 2015
  
- [2] Boolean algebra website: <https://www.boolean-algebra.com>